

Name: _____

Learning Target: I can show my understanding of how circuits work.

Date: _____

Circuits

Fill in the missing words.

loop

complete

energy

path

negative

positive

electricity

A circuit is a _____ that allows _____ to pass through it.

Electricity always travels from the _____ to the _____.

A circuit will only work if it is _____. This means it must make a complete _____, otherwise the electrical _____ cannot flow.

Draw arrows on the diagram to show which way the electricity is flowing.

