

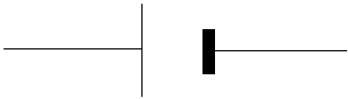
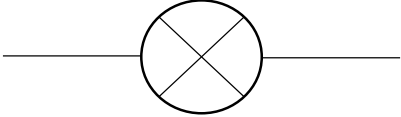

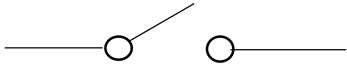

Name: _____

Learning Target: I can identify and draw circuit symbols.

Date: _____

Circuits

Electricity can provide light, heat, or mechanical energy.

SYMBOL	Can you copy the symbol?
 <p data-bbox="477 745 578 779">Battery</p>	
 <p data-bbox="500 982 581 1016">Lamp</p>	
 <p data-bbox="506 1209 571 1243">Wire</p>	
 <p data-bbox="451 1430 652 1463">Switch (open)</p>	
 <p data-bbox="444 1648 669 1682">Switch (closed)</p>	